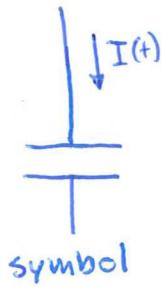


Capacitors

$$V_c = \frac{1}{C} \int I dt$$

equation



$C = [F] = [\text{Farad}]$

$$C = \left[\frac{\text{amp}^2 \text{s}^4}{\text{kg m}^2} \right]$$

units

if $I(t) = I_p \sin(\omega t - \phi_I)$

then: $V_c = \frac{1}{C} \int I_p \sin(\omega t - \phi_I) dt$

$$= \frac{-1}{WC} I_p \cos(\omega t - \phi_I)$$

$$V_c = \frac{1}{WC} I_p \sin(\omega t - \phi_I - \frac{\pi}{2})$$

in time domain V_c leads the current by 90°

move to complex plane:

$$V_c = \text{Im} \left(\frac{1}{WC} I_p e^{i(\omega t - \phi_I - \frac{\pi}{2})} \right)$$

$$= \text{Im} \left(\frac{1}{WC} I_p e^{i\omega t} e^{-i\phi_I} e^{-i\frac{\pi}{2}} \right)$$

$$= \text{Im} \left(\frac{-i}{WC} I_p e^{-i\phi_I} e^{i\omega t} \right)$$

move to phasor reference frame:

$$\text{Im} \left(\tilde{V}_c e^{i\omega t} \right) = \text{Im} \left(\frac{-i}{WC} \tilde{I} e^{i\omega t} \right)$$

rotating reference frame

where: $\tilde{V}_c = V_{c,p} e^{-i\phi_r}$ & $\tilde{I} = I_p e^{-i\phi_I}$

separate phasor part:

$$\tilde{V}_c = \frac{-i}{WC} \tilde{I}$$

$$V_c = Z_c \tilde{I}$$


in phase domain

where

$$Z_c = \frac{-i}{WC}$$

Z_c is Imaginary and is -90° to the real axis

$$-\cos(x) = \sin(x - \frac{\pi}{2})$$

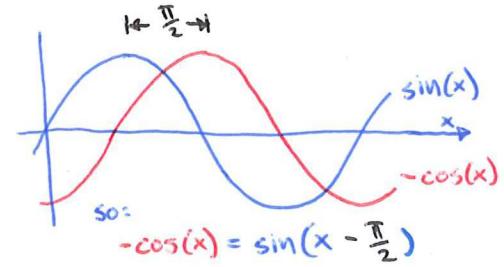


$$e^{i\theta} = \cos\theta + i\sin\theta$$

$$x^{m+n} = x^m x^n$$

$$e^{-i\frac{\pi}{2}} = -i$$

phasors

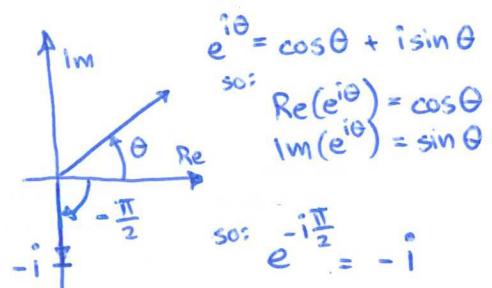

Phasors:

