

Resistors

$$V_R = IR$$

equation



symbol

$$R = [\Omega] = [\text{ohms}]$$

$$[\Omega] = \left[\frac{\text{kg m}^2}{\text{amp}^2 \text{s}^3} \right]$$

units


$$\text{if } I(t) = I_p \sin(\omega t - \phi_I)$$

then:

$$V_R = R I_p \sin(\omega t - \phi_I)$$

in time domain V_R is in phase with current.
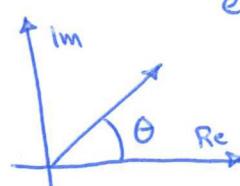
$$e^{i\theta} = \cos\theta + i\sin\theta$$



$$e^{i\theta} = \cos\theta + i\sin\theta$$

$$\text{so: } \text{Re}(e^{i\theta}) = \cos\theta \\ \text{Im}(e^{i\theta}) = \sin\theta$$

move to complex plane:

$$V_R = \text{Im} (R I_p e^{i(\omega t - \phi_I)})$$

$$x^{m+n} = x^m x^n$$

$$= \text{Im} (R I_p e^{i\omega t} e^{-i\phi_I})$$

$$= \text{Im} (R I_p e^{-i\phi_I} e^{i\omega t})$$

move to phasor reference frame:

$$\text{Im} (\tilde{V}_R e^{i\omega t}) = \text{Im} (R \tilde{I} e^{i\omega t})$$

↑ rotating reference frame

$$\text{where: } \tilde{V}_R = V_{R,p} e^{-i\phi_V} \text{ & } \tilde{I} = I_p e^{-i\phi_I}$$

separate phasor part:

$$\tilde{V}_R = R \tilde{I}$$

$$\tilde{V}_R = Z_R \tilde{I}$$

where

$$Z_R = R$$

in phase domain Z_R is Real

Phasors:

